

课程设计

实验指导

● 药片装瓶系统设计

● 电子钟

● 选做



知识准备



● 复习

《数字逻辑》 VHDL内容

通知



其他所有由各班实验老师安排。

实验内容

- 药片装瓶系统设计
- 电子钟；
- 自选实验由实验老师给定

资源占用

先设计、再仿真，看占用资源数，**Compilation Report→Fitter** 器件资源利用情况，引脚分配情况

Quartus II - D:/test/ls374 - ls374 - [Compilation Report - Fitter Summary]

File Edit View Project Assignments Processing Tools Window Help

ls374

Project Navigator

Entity	Combinational ALUTs	ALUTs	Dedicated logic registers
Stratix II: AUTO			
ls374	0 (0)	0 (0)	0

Hierarchy Files Design Units

Tasks

Task: Compilation

Task List

- Compile Design
- Analysis & Synthesis
- Fitter (Place & Route)
- Assembler (Generate programming files)
- Classic Timing Analysis
- EDA Netlist Writer
- Program Device (Open Programmer)

ls374.vhd

- Flow Elapsed Time
- Flow OS Summary
- Flow Log
- Analysis & Synthesis
 - Summary
 - Settings
 - Settings
- Source Files Read
- Resource Usage Summary
- Resource Utilization
- Optimization Results
- Messages
- Fitter**
 - Summary
 - Settings
 - Parallel Compilation
 - I/O Assignment Worksheet
 - Incremental Compilation
 - Pin-Out File
 - Resource Section

Compilation Report - Fitter Summary

Fitter Summary


Fitter Status	Successful - Tue Mar 01 14:55:03 2022
Quartus II Version	9.0 Build 235 06/17/2009 SP 2 SJ Web Edition
Revision Name	ls374
Top-level Entity Name	ls374
Family	Stratix II
Device	EP2S15F484C3
Timing Models	Final
Logic utilization	0 %
Combinational ALUTs	0 / 12,480 (0 %)
Dedicated logic registers	0 / 12,480 (0 %)
Total registers	0
Total pins	6 / 343 (2 %)
Total virtual pins	0
Total block memory bits	0 / 419,328 (0 %)
DSP block 9-bit elements	0 / 96 (0 %)
Total PLLs	0 / 6 (0 %)
Total DLLs	0 / 2 (0 %)

尽量少用多层嵌套的 if then else
编译之后，点击


Tool>>Netlist Viewers>>RTL Viewers

设计思路



自顶向下，逐级细化
采用结构化（模块化）设计思想

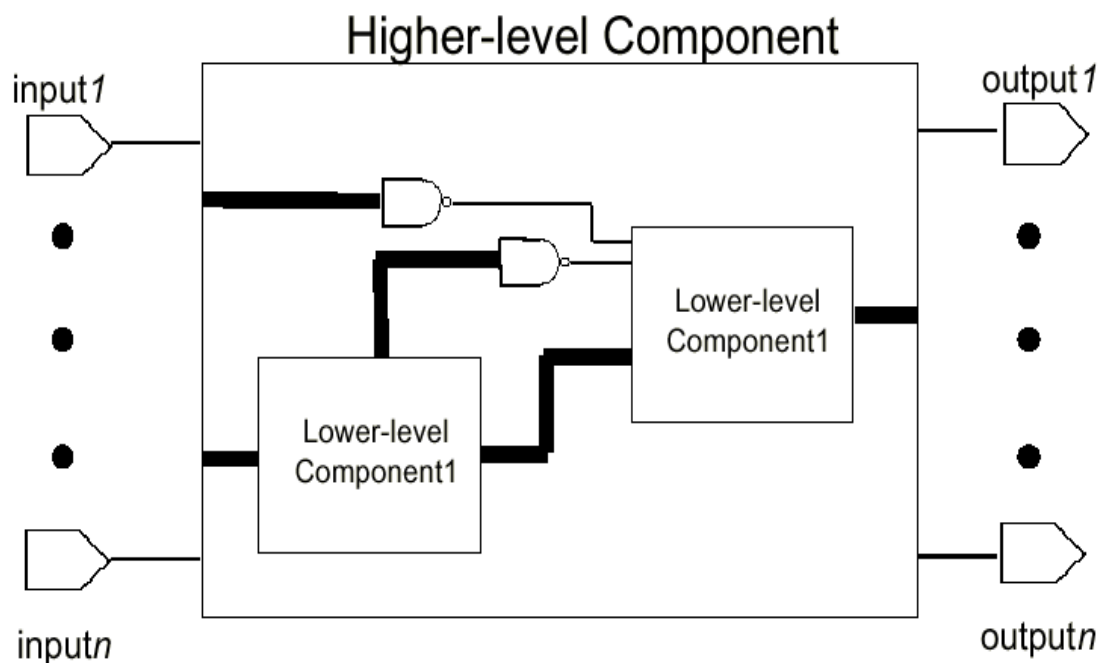


简易频率计

 


1S的闸门信号内计数的结果
就是被测信号的频率

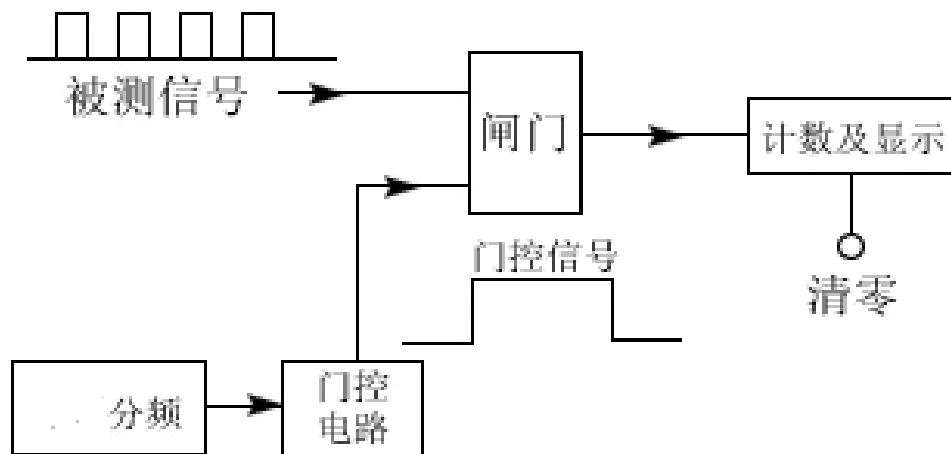 

 1. 产生准确闸门信号 (1s) 。
5kHz时钟经5000分频 (一次完成) ，再经2分频产生方波，1s用于计数，1s用于显示结果及清零) ；
2. 使能控制计数，计数结果寄存；
3. 每次对被测信号计数前，自动异步清零；
4. 计数器采用十进制；
5. 显示器有1个需要写显示译码功能，驱动7段发光管，其他5个直接输出8421码给显示器数码管高低位的接线。



Clk (1Hz)

 

计数使能信号 (高有效)



寄存信号 (上升沿有效)




清零信号 (高有效)



0.5S

频率计

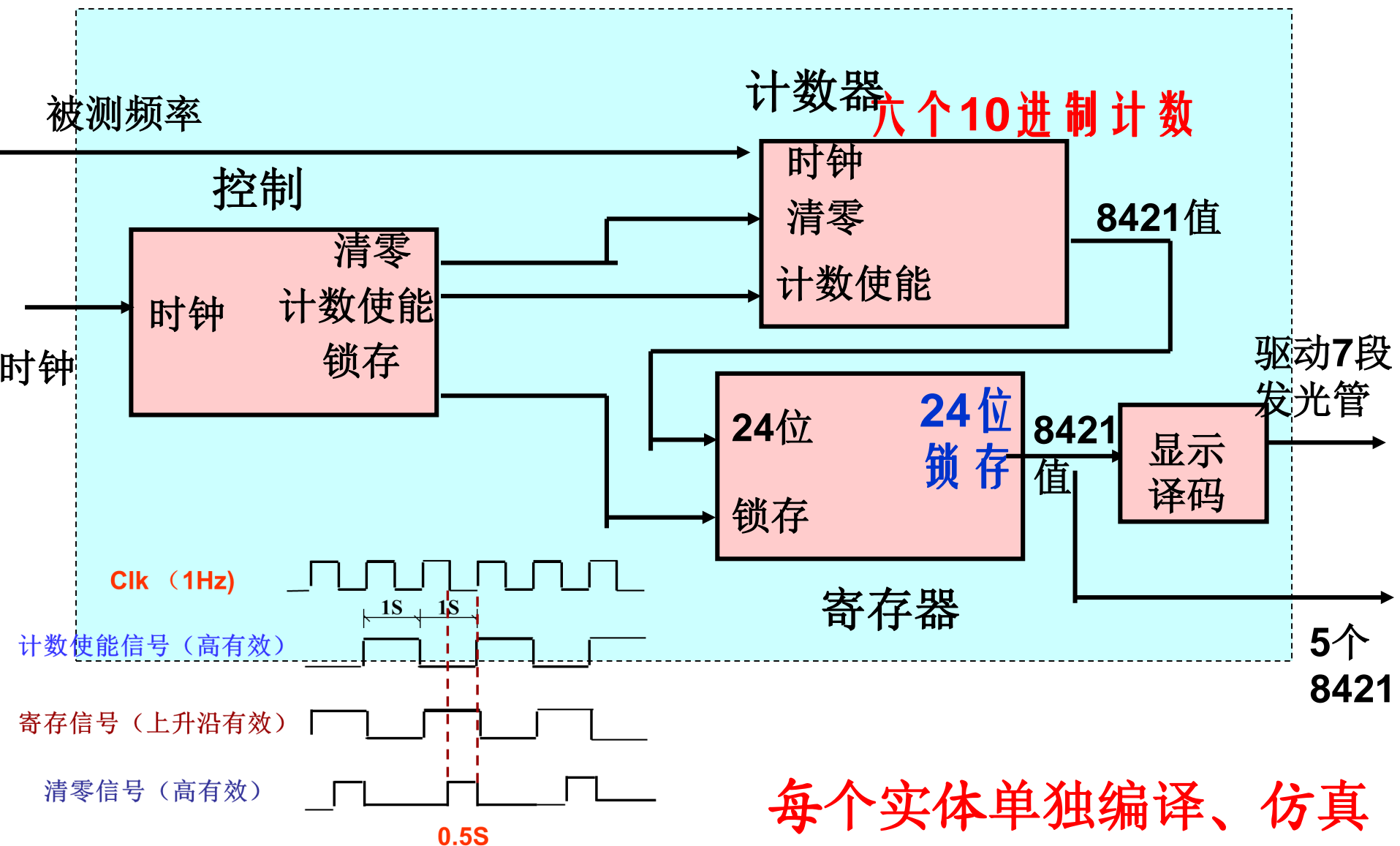

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;

```

```

ENTITY Data_fre_count IS
PORT(clk1:IN STD_LOGIC; --待测
    CLK: IN STD_LOGIC; --5KHz
    ledout1: OUT STD_LOGIC_VECTOR(6 DOWNT0 0); --驱动7段发光管
    ledout2: OUT STD_LOGIC_VECTOR(19 DOWNT0 0) -- 5个7段显示译码器
);

```

```

END Data_fre_count;
ARCHITECTURE func OF Data_fre_count IS

```

```

    COMPONENT divide1

```

```


    PORT(cp_50:IN STD_LOGIC;
        cp1:OUT STD_LOGIC; --使能
        cp2:OUT STD_LOGIC; --寄存
        cp3:OUT STD_LOGIC --清零
    );

```

```

END COMPONENT;


```

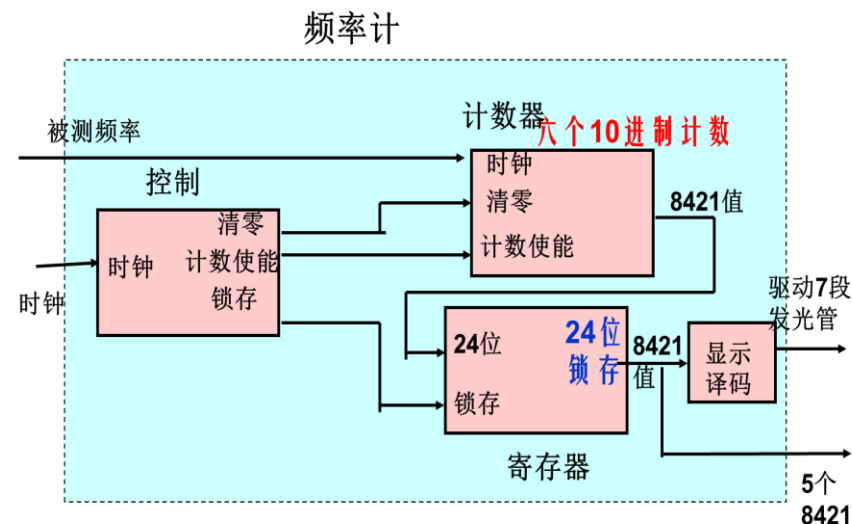

```

COMPONENT count10_6
    PORT(CLK:IN STD_LOGIC;
        EN: IN STD_LOGIC;
        CLR:IN STD_LOGIC;
        d:OUT STD_LOGIC_VECTOR(23 DOWNT0 0)
    );
END COMPONENT;

```

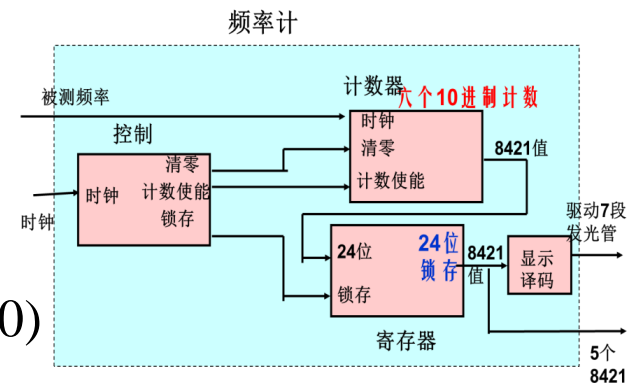

```

COMPONENT latch6
    PORT(lock:IN STD_LOGIC;
        qin: IN STD_LOGIC_VECTOR(23 DOWNT0 0);
        qout:OUT STD_LOGIC_VECTOR(23 DOWNT0 0)
    );
END COMPONENT;

```

```

COMPONENT display
    PORT( pin:IN STD_LOGIC_VECTOR(3 DOWNT0 0);
        pout:OUT STD_LOGIC_VECTOR(6 DOWNT0 0)
    );
END COMPONENT;

```

```


SIGNAL clr_1:STD_LOGIC;
SIGNAL c_gate:STD_LOGIC;
SIGNAL lock_1:STD_LOGIC;
SIGNAL g,h:STD_LOGIC_VECTOR(23 DOWNT0 0);
SIGNAL leds:STD_LOGIC_VECTOR(6 DOWNT0 0); --7段
BEGIN

u1:divide1 PORT MAP(CLK, c_gate, lock_1, clr_1);
u2:count10_6 PORT MAP(clk1, c_gate, clr_1, g);
u3:latch6 PORT MAP(lock_1, g, h);
u4:display PORT MAP(h(23 DOWNT0 20), leds);

ledout1<=leds;
ledout2<=h(19 DOWNT0 0);

END func;

```

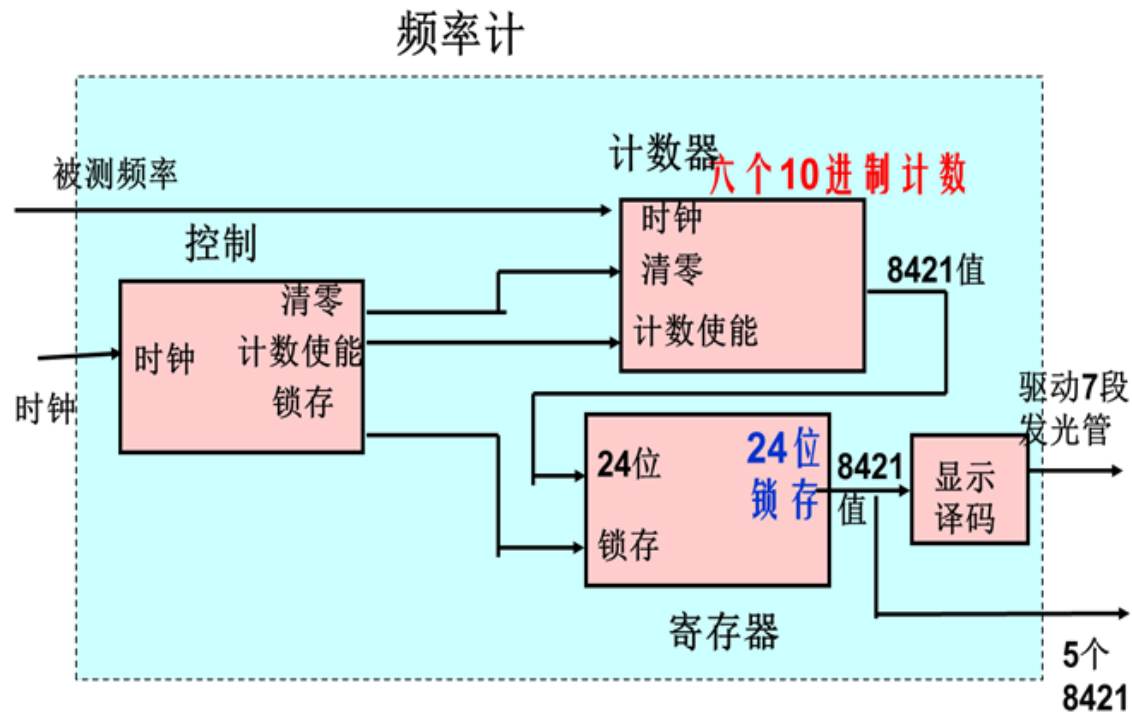

```

LIBRARY IEEE; --分频及控制模块
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;

```

```

ENTITY divide1 IS

```

```

    PORT(cp_50:IN STD_LOGIC;
          cp1:OUT STD_LOGIC; -- 0.5Hz使能
          cp2:OUT STD_LOGIC; --寄存
          cp3:OUT STD_LOGIC --清零
    );

```

```

END divide1;

```

```



ARCHITECTURE func OF divide1 IS

```

```

    SIGNAL temp: INTEGER RANGE 0 TO 5000;
    SIGNAL tout1:STD_LOGIC; --1HZ方波
    SIGNAL tout2:STD_LOGIC;

```

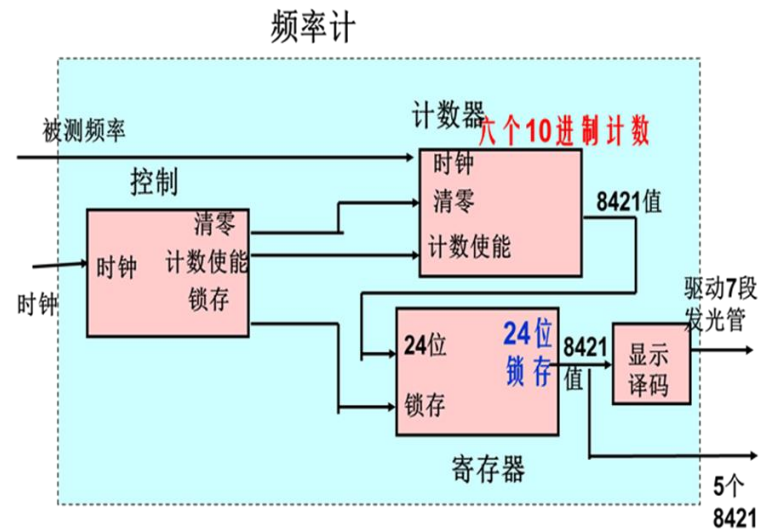 

```
BEGIN
```

```
p1:PROCESS(cp_50)
```

--5000分频

```
BEGIN
```

```
IF(cp_50'event AND cp_50='1')THEN
```

```
IF temp=4999 THEN
```

```
temp <= 0;
```

```
else
```

```
temp <= temp+1;
```

```
END IF;
```

```
END IF;
```

```
END PROCESS;
```

```
p2:PROCESS(cp_50,temp)
```

```
BEGIN
```

```
IF(cp_50'event AND cp_50='1')THEN
```

```
if( temp<2500) then
```

```
tout1 <= '1' ; --1Hz方波
```

```
else
```

```
tout1 <= '0';
```

```
end if;
```

```
END IF;
```

```
END PROCESS;
```

tout1


Clk (1Hz)

计数使能信号 (高有效)

寄存信号 (上升沿有效)

清零信号 (上升沿有效)

0.5S

 

p3:PROCESS(tout1) --2分频，0.5Hz方波

VARIABLE t:STD_LOGIC;

BEGIN

IF(tout1'event AND tout1='1')THEN --作为时钟信号、计数使能、打入脉冲，不能有竞争冒险

t := NOT t;

IF(t='1')THEN

cp1<='1'; --计数使能，高电平

cp2<='0'; --寄存，上升沿

ELSE

cp1<='0';

cp2<='1';

END IF;

END IF;

END PROCESS;

P4:PROCESS(tout1,cp1)

BEGIN

IF(tout1='0'AND cp1='0')THEN


cp3<='1'; --清零

ELSE

cp3<='0';

END IF;

END PROCESS; END func;

 

```

LIBRARY IEEE; --24位锁存器模块
USE IEEE.STD_LOGIC_1164.ALL;

```

```



ENTITY latch6 IS
PORT( lock:IN STD_LOGIC;
      qin: IN STD_LOGIC_VECTOR(23 DOWNTO 0);
      qout:OUT STD_LOGIC_VECTOR(23 DOWNTO 0)
);
END latch6;

```

```

ARCHITECTURE func OF latch6 IS
    SIGNAL temp:STD_LOGIC_VECTOR(23 DOWNTO 0);
BEGIN
    PROCESS(lock)
    BEGIN
        IF lock'event AND lock='1' THEN
            temp<=qin;
        END IF;
        qout<=temp;
    END PROCESS;
END func;

```

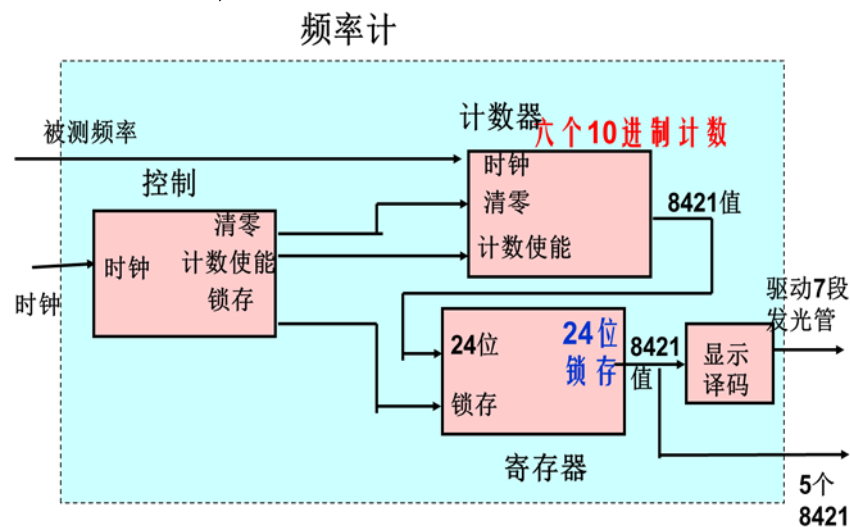 


```
LIBRARY IEEE; --10进制计数器 0--9
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
ENTITY count10 IS
    PORT(CLK:IN STD_LOGIC;
          EN: IN STD_LOGIC;
          CLR:IN STD_LOGIC;
          qout:OUT STD_LOGIC_VECTOR(3 DOWNT0 0);
          cout:OUT STD_LOGIC
    );
END count10
```

```
ARCHITECTURE func OF count10 IS
    SIGNAL temp:STD_LOGIC_VECTOR(3 DOWNT0 0);
BEGIN
```



```

BEGIN
  PROCESS(CLK,EN,CLR)
  BEGIN
    IF(CLR='1')THEN
      temp<="0000";  --异步清零
    ELSIF(EN='1')THEN  --计数使能
      IF (CLK'event AND CLK='1')THEN
        IF(temp="1001")THEN
          temp<="0000";
          cout<='1' ;  --寄存的进位输出，给高一级提供计数时钟
        ELSE
          temp<=temp+1;
          cout <= '0';
        END IF;
      END IF;
    END IF;
  END PROCESS;
  qout<=temp;
END func;

```



LIBRARY IEEE; --6个10进制计数器 (000000~999999)

USE IEEE.STD_LOGIC_1164.ALL;

USE IEEE.STD_LOGIC_UNSIGNED.ALL;

ENTITY count10_6 IS

PORT(CLK:IN STD_LOGIC;

EN: IN STD_LOGIC;

CLR:IN STD_LOGIC;

d:OUT STD_LOGIC_VECTOR(23 DOWNT0 0)

);

END count10_6;

ARCHITECTURE func OF count10_6 IS

COMPONENT count10

PORT(CLK:IN STD_LOGIC;

EN: IN STD_LOGIC;


CLR:IN STD_LOGIC;

qout:OUT STD_LOGIC_VECTOR(3 DOWNT0 0);

cout:OUT STD_LOGIC

);

END COMPONENT;

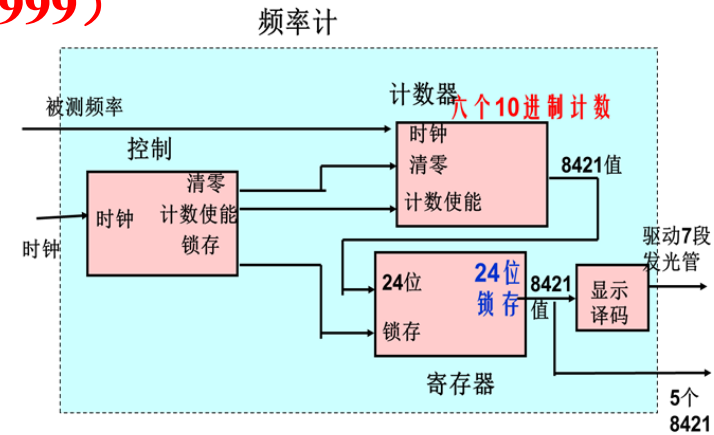

```
SIGNAL c:STD_LOGIC_VECTOR(6 DOWNT0 0);
```

```
BEGIN
```

```
u1:count10 PORT MAP(CLK, EN,CLR, d(3 DOWNT0 0),c(0));
```

```
u2:count10 PORT MAP(c(0), EN,CLR, d(7 DOWNT0 4),c(1));
```


```
u3:count10 PORT MAP(c(1), EN,CLR, d(11 DOWNT0 8),c(2));
```

```
u4:count10 PORT MAP(c(2), EN,CLR, d(15 DOWNT0 12),c(3));
```

```
u5:count10 PORT MAP(c(3), EN,CLR, d(19 DOWNT0 16),c(4));
```

```
u6:count10 PORT MAP(c(4), EN,CLR, d(23 DOWNT0 20),c(5));
```

```
END func;
```

 

LIBRARY IEEE; **--7段显示译码**

USE IEEE.STD_LOGIC_1164.ALL;

USE IEEE.STD_LOGIC_UNSIGNED.ALL;

ENTITY display IS

PORT(pin:IN STD_LOGIC_VECTOR(3 DOWNT0 0);

pout:OUT STD_LOGIC_VECTOR(6 DOWNT0 0));

END display;

ARCHITECTURE func OF display IS

BEGIN

process(pin)

begin

case pin is

when "0000" => pout<="0111111" ;

ween "0001" => pout<= "0000110";

when "0010" => pout<="1011011" ;

when "0011" => pout<="1001111" ;

when "0100" => pout<="1100110" ;

when "0101" => pout<="1101101" ;

when "0110" => pout<="1111101" ;

when "0111" => pout<="0000111" ;


when "1000" => pout<="1111111" ;

when "1001" => pout<="1101111" ;

end case ;

end process;


END func;

 


药片装瓶系统



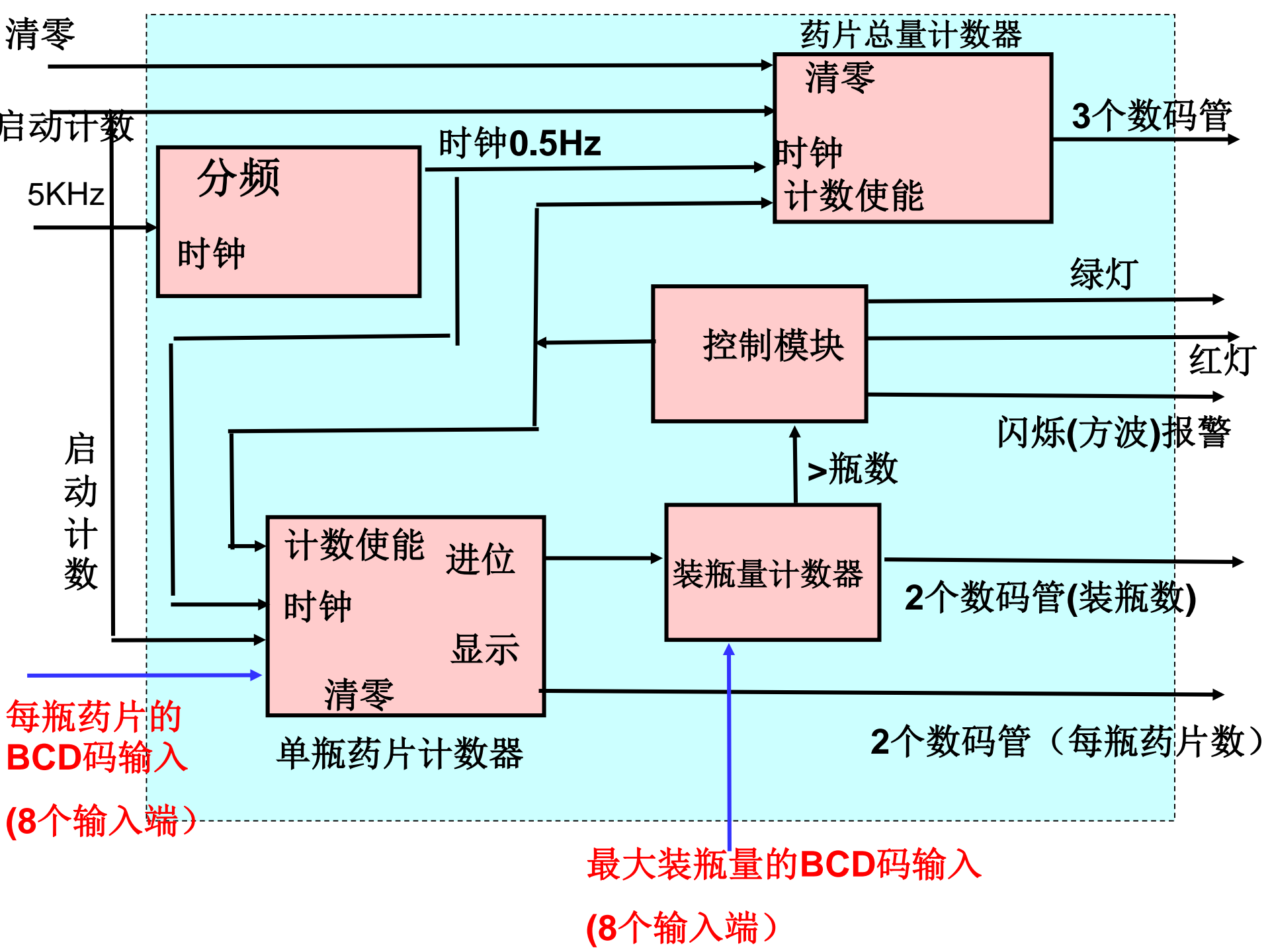- **BCD码**每瓶装药数输入，要求每瓶最大药片数**50**粒，最多装**18**瓶。
- 药片：**0.5Hz**方波
- 超过设定瓶数报警。
- 绿灯：正在装瓶。
- 红灯：装瓶停止。
- 启动：**=0**设置两个初值；**=1**装瓶



电子钟显示

 

顶层模块(
clock)

底层模块(
clk_ring)

提供1Hz和整点响铃脉冲

底层模块(
cnt60)

60进制计数器

底层模块(
cnt24)

24进制计数器

底层模块(
encode24)

2-4译码器

底层模块(
ring)

整点响铃信号

(1) 时钟各组成计数器的设计。最基本的为1s 计时器，通过对输入脉冲5KHZ 时钟信号二次分频得到。其次由于时钟的分和秒为60 进制，小时为24 进制，故设置60 计数器counter_60和24 进制的计数器counter_24。

(2) 元件连接模块。分频得到的1s计时器的时钟脉冲sec给控制秒的60进制计数器，控制秒的60进制计数器进位c0给控制分钟的60进制计数器，进而进位给24进制计数器，并将得到的相应的时、分、秒信号与对应的输出d1、d10相连（最高位为7段译码），最后通过数码管显示。

(3) 控制信号。首先是清零信号，采用了电平的有效方式。其次是调表控制信号，采用信号change上升沿触发的方式改变修改模式，并用相同方式对时钟修改，模式mode采用了 2—4译码器：“00”为正常工作状态，“01”状态下对小时进行修改，“10”状态下对分钟进行修改，“11”状态下对秒进行修改。

(4) 完成报时功能，通过分钟向小时的进位来产生响铃的控制信号，此信号持续一分钟，将响铃信号控制在四秒，前三秒为低音C后一秒为高音C。此外，为了达到到特定的响铃效果，响铃进程采用50KHZ的时钟信号控制响铃的音调，并将其二分频以提高响度。

PROCESS(clk,clr) --24进制计数器

BEGIN

IF(clr='0')THEN

temp1<="0000";

temp10<="0000";

ELSIF(clk'event AND clk='1')THEN

IF(temp1=3 AND temp10=2)THEN

temp1<="0000";

temp10<="0000";

ELSIF(temp1=9)THEN

temp1<="0000";

temp10<=temp10+1;

ELSE

temp1<=temp1+1;

END IF;

END IF;

END PROCESS;

PROCESS(clk,clr) --60进制计数器

BEGIN

IF(clr='0')THEN

temp1<="0000";

temp10<="0000";

ELSIF(clk'event AND clk='1')THEN

IF(temp1=9)THEN

temp1<="0000";

IF(temp10=5)THEN

temp10<="0000";

co_temp<='1'; --给高一级的时钟

ELSE

temp10<=temp10+1;

co_temp<='0';

END IF;

ELSE

temp1<=temp1+1;

co_temp<='0';

END IF;

END IF;

END PROCESS;